

$$\begin{aligned}
 Q1) \quad \hat{i}_L(t) &= \frac{1}{L} \int_0^t v_L(t) dt + \hat{i}_L(0) \\
 &= \frac{1}{10 \times 10^{-6}} \int_0^t 20 dt - 200 \times 10^{-3}
 \end{aligned}$$

$$\hat{i}_L(t) = 20 t 10^5 - 200 \times 10^{-3}$$

$$200 \times 10^{-3} = 20 t 10^5 - 200 \times 10^{-3}$$

$$400 \times 10^{-3} = 20 t 10^5$$

$$\begin{aligned}
 t_x &= \frac{400 \times 10^{-3}}{20 \times 10^5} = 20 \times 10^{-8} \text{ A} \\
 &= \boxed{0,2 \mu\text{s}}
 \end{aligned}$$

Q2) the switch is closed at  $t=0^-$ , therefore initial voltage is zero

$$\begin{aligned}
 V(t) &= \frac{1}{C} \int \hat{i}(t) dt + V(0) \Rightarrow 10^{-5} \int_0^t (2 \times 10^{-3}) dt + 0 \\
 &= 200 t
 \end{aligned}$$

$$\text{at } t = 10 \text{ ms} \quad V(10 \times 10^{-3}) = \boxed{2 \text{ V}}$$

$$P = V \cdot \hat{i} = 0,4 \text{ t}$$

$$P(10 \times 10^{-3}) = \boxed{4 \text{ mW}}$$

$$w(t) = \frac{1}{2} C \cdot v^2(t) = 0,2 t^2$$

$$w(10 \times 10^{-3}) = \boxed{20 \text{ mJ}}$$

$$Q3) \quad 2e^{-3t} = \frac{V_c(t)}{R} + C \cdot \frac{dV_c(t)}{dt}$$

particular solution  $V_{cp}(t) = A \cdot e^{-3t}$

$$2e^{-3t} = \frac{A}{R} e^{-3t} - 3AC e^{-3t}$$

$$R = 1 \text{ M}\Omega = 10^6 \Omega$$

$$C = 1 \times 10^{-6} \text{ F}$$

$$2e^{-3t} = \frac{A}{10^6} e^{-3t} - 3 \cdot A \cdot 10^{-6} e^{-3t}$$

$$2e^{-3t} = e^{-3t} \left( \frac{A}{10^6} - 3A \cdot 10^{-6} \right)$$

$$= e^{-3t} (A \cdot 10^{-6} - 3A \cdot 10^{-6})$$

$$= e^{-3t} (-2A \cdot 10^{-6})$$

$$A = -10^6$$

$$V_c(t) = V_{\text{particular}} + V_{\text{comp}}$$

$$= -10^6 e^{-3t} + K_1 e^{-t/\tau}$$

$$V_c(0^+) = 0 \quad \& \quad \tau = RC = 1$$

$$V_c(0^+) = -10^6 + K_1 = 0 \Rightarrow K_1 = 10^6$$

General solution  $V_c(t) = 10^6 e^{-t} - 10^6 e^{-3t}$

$$Q4) \quad \underbrace{(5 \cdot \cos(10t))}_{df} = \underbrace{\left( \frac{V(t)}{10} \right)}_{df} + \underbrace{\left( \int_0^t V(t) dt + i_L(0) \right)}_{df}$$

→ After writing KCL, we differentiate each term wrt time

$$-50 \cdot \sin(10t) = \frac{1}{10} \frac{dV(t)}{dt} + V(t)$$

$$V_p = A \cdot \cos(10t) + B \cdot \sin(10t) \rightarrow \text{substitute into solution.}$$

$$-50 \cdot \sin(10t) = \frac{1}{10} [-10A \sin(10t) + 10B \cos(10t)] + [A \cos(10t) + B \sin(10t)]$$

the cosine coefficients should be zero on the right hand side and sine coefficients should be  $-50$

$$\begin{aligned} -50 &= -A + B \\ 0 &= B + A \end{aligned} \quad \Rightarrow \quad \begin{aligned} A &= 25 \\ B &= -25 \end{aligned}$$

$$V(t) = V_{\text{particular}} + V_{\text{complementary}} \\ = V_p(t) + K_1 \cdot e^{-t/\tau}$$

$\tau$  = time constant for RL circuit

$$\tau = \frac{L}{R} = 0.1 \text{ sec.}$$

$$= 25 \cdot \cos(10t) - 25 \cdot \sin(10t) + K_1 \cdot e^{-10t}$$

current of inductor at  $t=0^+$  is zero  $i_L(0^+) = 0$

at  $t=0^+$  all current goes through Resistor

$$\text{at } t=0^+ \quad i_R(0^+) = 5A \Rightarrow v_R(0^+) = 5 \times 10 = 50V$$

therefore

$$50 = 25 \cdot \cos(0) - 25 \cdot \sin(0) + K_1 \cdot e^{-0}$$

therefore

$$50 = 25 \cdot \cos(0) - 25 \cdot \sin(0) + K_1 \cdot 1$$

$$K_1 = 25$$

$$V(t) = 25e^{-10t} + 25 \cos(10t) - 25 \sin(10t)$$


Q5) Steady state representations for L & C

L  $\rightarrow$  short circuit

C  $\rightarrow$  open circuit


prior to  $t=0$  (before switch opens)

the circuit can be represented as:

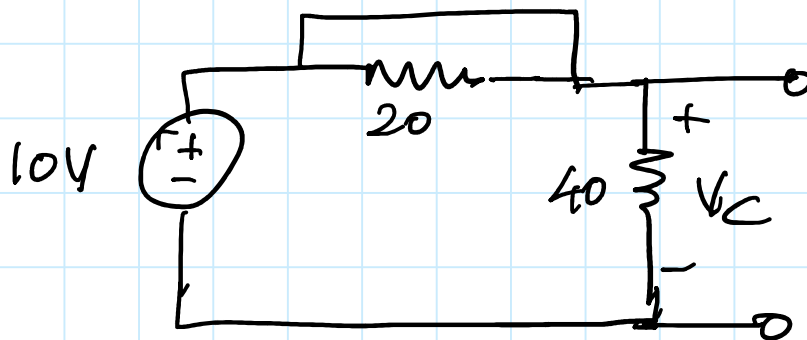

$$V_C = 10V$$

after  $t > 0$  the circuit becomes

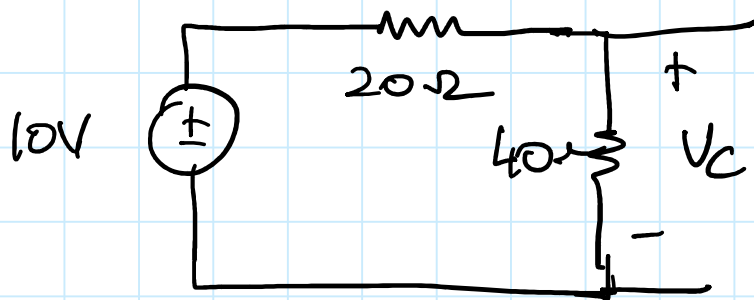

$$V_C = 10 \cdot \frac{40}{40 + 20}$$

$$V_C = 6.66$$

Q6) using KVL we obtain:

$$L \cdot \frac{d\hat{i}_s(t)}{dt} + R \cdot \hat{i}_s(t) = 15 \cdot \cos(300t)$$

$$2. \frac{d\hat{i}_s(t)}{dt} + 300 \hat{i}_s(t) = 15 \cdot \cos(300t)$$

particular solution given in the hint!

$$\hat{i}_{sp} = A \cdot \cos(300t) + B \cdot \sin(300t)$$

substitute  $\hat{i}_{sp}$  into eqn:

$$\frac{d\hat{i}_{sp}(t)}{dt} = -300A \sin(300t) + 300B \cos(300t)$$

$$-600A \sin(300t) + 600B \cos(300t) + 300A \cos(300t) + 300B \sin(300t) = 15 \cdot \cos(300t)$$

coefficients of sines  $\rightarrow 0$   
of cosines  $\rightarrow 15$

$$-600A + 300B = 0 \quad \rightarrow 300B = 600A$$

$$600B + 300A = 15 \quad B = 2A$$

$$\rightarrow 1200A + 300A = 15 \quad -2$$

$$1500A = 15 \rightarrow A = 10^{-2}$$

$$B = 2 \times 10^{-2}$$

$$\hat{i}_s(t) = \hat{i}_s^{\text{complementary}} + \hat{i}_s^{\text{particular}}$$

$$\hat{i}_{sc} = k_1 \cdot e^{-t/\tau} \rightarrow k_1 \cdot e^{-Rt/L} = k_1 \cdot e^{-150t}$$

$$\hat{i}_{sc}(t) = k_1 \cdot e^{-150t} + 10^{-2} \cos(300t) + 2 \cdot 10^{-2} \sin(300t)$$

Current across  $L$  cannot change instantaneously  
therefore  $\hat{i}_s(0^+) = 0 \rightarrow$  substitute into eqn to find  $k_1$

$$\hat{i}_s(0) = 0 = k_1 + 10^{-2} \Rightarrow k_1 = -10^{-2}$$

the solution is

$$\hat{i}_s(t) = -10^{-2} e^{-150t} + 10^{-2} \cos(300t) + 2 \cdot 10^{-2} \sin(300t)$$